

B.Sc. (HONS.) in ECE  
**Part-III, Sixth Semester Examination – 2020**  
**Subject:** Industrial and Power Electronics (ECE-313)  
**Duration:** 3 Hours  
**Full Marks:** 80

*[N.B. The figures in the right margin indicate full marks. Answer any five questions.]*

	Marks
--	-------

### **Question 1**

**(a) What is a transducer? What are the basic constituent elements of a transducer? (4 Marks)**

A **transducer** is a device that converts one form of energy into another, typically physical quantities into electrical signals.

**Constituent Elements:**

1. **Sensing Element** – Detects the physical quantity.
2. **Transduction Element** – Converts sensed quantity into electrical signal.
3. **Signal Conditioning Unit** – Amplifies/modifies the signal.
4. **Output Device** – Displays or transmits the signal.

**(b) Define temperature. Differentiate between active and passive transducer. (6 Marks)**

**Temperature** is the measure of the average kinetic energy of particles in a substance, indicating its thermal state.

**Active Transducer:**

- Generates output without external power.
- Example: Thermocouple.

**Passive Transducer:**

- Requires external power to operate.
- Example: RTD (Resistance Temperature Detector).
- 

Feature	Active Transducer	Passive Transducer
Power Requirement	No	Yes
Output Signal	Self-generated	Needs excitation
Example	Thermocouple	RTD

**(c) What is Zener diode? Write down the advantages and disadvantages of thermocouple. (6 Marks)**

A **Zener diode** is a semiconductor device that allows current to flow in reverse direction when the voltage exceeds a specific value (Zener breakdown voltage).

**Advantages of Thermocouple:**

- Wide temperature range.
- Fast response.
- Rugged and simple.

**Disadvantages:**

- Non-linear output.
- Requires reference junction.
- Low output voltage.

**Question 2**

**(a) Operation and I-V characteristics of SCR (6 Marks)**


**SCR (Silicon Controlled Rectifier)** is a four-layer, three-terminal device used for switching.

**Operation:**

- Remains OFF until gate is triggered.
- Once ON, conducts until current drops below holding value.
- 

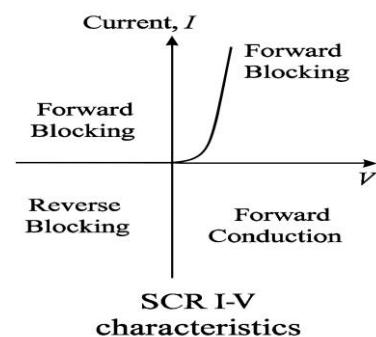**I-V Characteristics:**

- Forward Blocking Region
- Forward Conduction Region
- Reverse Blocking Region



📌 *Diagram: Show I-V curve with regions labeled.*

**(b) Ways of thyristor turn-on (4 Marks)**

1. **Gate Triggering** – Applying gate pulse.
2. **Voltage Triggering** – Increasing forward voltage.
3. **dv/dt Triggering** – Rapid voltage change.
4. **Temperature Triggering** – Heating junction.

### (c) Gauge Factor of Strain Gauge (6 Marks)

**Gauge Factor (GF)** is defined as:

$$[ GF = \frac{\Delta R}{R} / \varepsilon ]$$

Where:

- ( $\Delta R$ ) = Change in resistance
- ( $R$ ) = Original resistance
- ( $\varepsilon$ ) = Strain

It represents sensitivity of strain gauge to mechanical deformation.

### Question 3

#### (a) What is thyristor? Explain operation principle with figure (6 Marks)

A **thyristor** is a four-layer (PNPN), three-terminal device used for power control.

#### Operation:

- Forward biased but OFF until gate is triggered.
- After triggering, conducts until current drops below holding level.

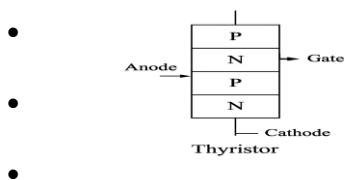


Diagram: Show thyristor layers and terminals.

#### (b) Applications of SCR (4 Marks)

- Motor speed control
- Light dimming
- Battery chargers
- Controlled rectifiers
- Overvoltage protection

#### (c) Schottky Diode and its Operation (6 Marks)

A **Schottky diode** is a metal-semiconductor junction diode with low forward voltage drop and fast switching.

#### Operation:

- Electrons flow from semiconductor to metal.


- No minority carrier storage → fast recovery.
- Used in high-speed switching and RF applications.

#### **Question 4**
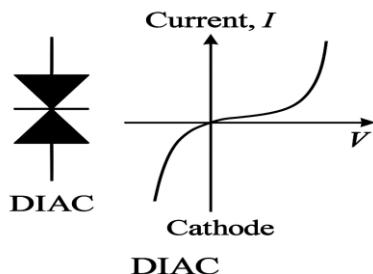
##### **(a) Operating Principle of DIAC (4 Marks)**

A DIAC is a bidirectional device that conducts only after reaching breakdown voltage in either direction.

- Once triggered, it conducts until current drops below holding value.
- Commonly used to trigger TRIACs.



.

→ *Diagram: DIAC symbol and V-I characteristics.*

##### **(b) Step-Up DC Chopper Operation (6 Marks)**

**Step-Up Chopper** increases output voltage above input.

#### **Working:**


- Switch ON → Inductor stores energy.
- Switch OFF → Inductor releases energy to load.

$$[ V_o = \frac{V_{in}}{1 - D} ]$$

Where (  $D$  ) = Duty cycle.
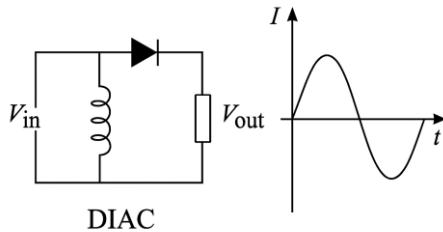
##### **(c) Single-Phase Full Wave Converter (6 Marks)**

- Converts AC to DC using two thyristors or diodes.
- Both halves of AC cycle are used.
- Output is pulsating DC with higher average voltage.



• *Diagram: Circuit and waveform.*

### Question 5

#### (a) Four Quadrant Converter (4 Marks)

Allows control of voltage and current in both directions.

**Quadrants:**

1. Forward Motoring
2. Forward Braking
3. Reverse Motoring
4. Reverse Braking

Used in regenerative motor drives.

#### (b) For $\alpha = \pi/2$ in Half-Wave Converter (6 Marks)

**(i) Efficiency:**

$$[\eta \approx 40.5\%]$$

**(ii) Form Factor:**

$$[FF \approx 1.57]$$

**(iii) Ripple Factor:**

$$[RF = \sqrt{FF^2 - 1} \approx 1.17]$$

#### (c) Programmable UJT (2 Marks)

A **PUT (Programmable UJT)** is a four-layer device whose characteristics can be adjusted using external resistors.

Used in timing and triggering applications.

#### (d) PLL Control of DC Drives (4 Marks)

**Phase-Locked Loop (PLL)** synchronizes motor speed with reference signal.

- Compares phase of feedback and reference.
- Adjusts control signal to maintain speed.

## ✓ Question 6

### (a) PLL Control Principle (6 Marks)

PLL uses:

- **Phase Detector** – Compares input and feedback.
- **Low-Pass Filter** – Removes high-frequency noise.
- **Voltage-Controlled Oscillator (VCO)** – Adjusts output frequency.

Maintains constant speed under load variations.

### (b) Fourth Quadrant Converter (4 Marks)

Operates in reverse voltage and reverse current mode.

- Enables regenerative braking.
- Power flows from load to source.

### (c) Cycloconverter and Single-Phase Cycloconverter (6 Marks)

**Cycloconverter** converts AC of one frequency to AC of another (usually lower).

**Single-Phase Cycloconverter:**

- Uses controlled switches to synthesize output.
- Suitable for low-speed, high-power applications.
- 

📌 *Diagram: Basic circuit and waveform.*

## ✓ Question 7 – Short Notes (Any Four × 4 = 16 Marks)

### (i) TRIAC

- Bidirectional thyristor.
- Controls AC power.

- Triggered by gate in both directions.
- Used in dimmers and motor control.

### (ii) PWM Inverter

- Converts DC to AC using Pulse Width Modulation.
- Controls output voltage and frequency.
- High efficiency and low harmonic distortion.

### (iii) Optical Transducer

- Converts light into electrical signal.
- Examples: Photodiodes, phototransistors.
- Used in encoders, sensors.

### (iv) Schottky Diode

- Metal-semiconductor junction.
- Low forward voltage drop ( $\sim 0.2\text{--}0.3\text{V}$ ).
- Fast switching, used in RF and power circuits.

### (v) Microprocessor-Based Motor Drive

- Uses microprocessor for control logic.
- Enables precise speed and torque control.
- Supports feedback and programmable settings.

### (vi) Silicon Bilateral Switch (SBS)

- Similar to DIAC but with gate terminal.
- Switches ON in both directions.
- Used in triggering TRIACs.

